

Table 1

	ad	ae	af	bcd	bce	bcf	de	df
ad	-	$d + e$	$d + f$	$a + bc$	$ad + bce$	$ad + bcf$	$a + e$	$a + f$
ae		-	$e + f$	$ae + bcd$	$a + bc$	$ae + bcf$	$a + d$	$ae + df$
af			-	$af + bcd$	$af + bce$	$a + bc$	$af + de$	$a + d$
bcd				-	$d + e$	$d + f$	$bc + e$	$bc + f$
bce					-	$e + f$	$bc + d$	$bce + df$
bcf						-	$bcf + de$	$bc + d$
de							-	$e + f$
df								-

(b) Two-cube divisors contain:

- (1) Directly obtained from Table 1: $\{d + e, d + f, e + f, a + bc, ae + bcd, af + bcd, ad + bcd, af + bce, ad + bcf, ae + bcf, a + e, a + d, af + de, bc + e, bc + d, bcf + de, a + f, ae + df, bc + f, bce + df\}$
- (2) Complement of (1): $\{a'b' + a'c', b'e' + c'e', b'd' + c'd', b'f' + c'f'\}$
- (3) Complement of (4): $\{a' + d', a' + e', a' + f', b' + c', b' + d', c' + d', b' + e', c' + e', b' + f', c' + f', d' + e', d' + f'\}$

Two-literal cube divisors contain:

- (4) Directly obtained from F : $\{ad, ae, af, bc, bd, cd, be, ce, bf, cf, de, df\}$
- (2) Complement of (1): $\{d'e', d'f', e'f', a'e', a'd', a'f'\}$

None of the two-cube divisors are kernels because all kernels listed in (a) have more than two cubes.

(c)

Step 1. Do $\text{GFACTOR}(F)$ to make $F = D_0Q_0 + R_0$.

We select $D_0 = a + bc + e + f$. Then $Q_0 = F/D_0 = d$. Since $|Q_0| = 1$, we shall return $\text{LF}(F, Q_0)$.

Step 2. Do $\text{LF}(F, Q_0)$ to make $F = D_1Q_1 + R_1$.

We select $L_1 = d$ and compute $(Q_1, R_1) = F/L_1 = (a + bc + e + f, ae + af + bce + bcf)$. We note that Q_1 is cube-free. Therefore, we recursively compute $\text{GFACTOR}(Q_1)$ and $\text{GFACTOR}(R_1)$. We note that Q_1 has no more non-trivial divisors, so only $\text{GFACTOR}(R_1)$ is required. Then we shall return $F = L_1Q_1 + \text{GFACTOR}(R_1)$.

Step 3. Do $\text{GFACTOR}(R_1)$ to make $R_1 = D_2Q_2 + R_2$.

We select $D_2 = e + f$. Then $Q_2 = R_1/D_2 = a + bc$. Since $|Q_2| \neq 0$ and Q_2 is already cube-free, we overwrite $(D_2, R_2) = (R_1/D_2, 0) = (e + f, 0)$. Then we recursively compute $\text{GFACTOR}(Q_2)$, $\text{GFACTOR}(D_2)$, and $\text{GFACTOR}(R_2)$. We note that Q_2 , D_2 , and R_2 have no more non-trivial divisors. Therefore, we return $R_1 = D_2Q_2 + R_2$.

Therefore,

$$\begin{aligned}
F &= \text{GFACTOR}(F) \\
&= \text{LF}(F, Q_0) \\
&= L_1Q_1 + \text{GFACTOR}(R_1) \\
&= d(a + bc + e + f) + (e + f)(a + bc).
\end{aligned}$$

- (d) Step 1. Do GFACTOR(F) to make $F = D_0Q_0 + R_0$.
 We select $D_0 = bc + d$. Then $Q_0 = F/D_0 = e + f$. Since $|Q_0| \neq 0$ and Q_0 is already cube-free, we overwrite $(D_0, R_0) = F/Q_0 = (a+bc+d, ad+bcd)$. Then we recursively compute GFACTOR(Q_0), GFACTOR(D_0), and GFACTOR(R_0). We note that Q_0 and D_0 have no more non-trivial divisors, so only GFACTOR(R_0) is required.
- Step 2. Do GFACTOR(R_0) to make $R_0 = D_1Q_1 + R_1$.
 We select $D_1 = a + bc$. Then $Q_1 = F/D_1 = d$. Since $|Q_1| = 1$, we shall return LF(R_0, Q_1).
- Step 3. Do LF(R_0, Q_1) to make $R_0 = D_2Q_2 + R_2$.
 We select $L_2 = d$ and compute $(Q_2, R_2) = F/L_2 = (a + bc, 0)$. We note that Q_2 is cube-free. Therefore, we recursively compute GFACTOR(Q_2) and GFACTOR(R_2). We note that Q_2 and R_2 have no more non-trivial divisors. Therefore, we return $R_0 = L_2Q_2 + R_2$.
- Therefore,

$$\begin{aligned}
 F &= \text{GFACTOR}(F) \\
 &= Q_0D_0 + \text{GFACTOR}(R_0) \\
 &= Q_0D_0 + \text{LF}(R_0) \\
 &= (e + f)(a + bc + d) + d(a + bc).
 \end{aligned}$$

3 [Extraction and Rectangle Covering]

The level-0 kernels and co-kernels of F are as follows.

Kernel	Co-kernel
$bc + ef$	$\{a, d\}$
$a + d$	$\{bc, ef\}$

The level-0 kernels and co-kernels of G are as follows.

Kernel	Co-kernel
$d + e$	ab
$bd + e$	ac
$bc + ef$	ad
$a + c + df$	ae
$ac + f$	bd
$ab + f$	cd
$ae + b + c$	df

Table 2

		<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>ab</i>	<i>ac</i>	<i>ae</i>	<i>bc</i>	<i>bd</i>	<i>cd</i>	<i>df</i>	<i>ef</i>
<i>F</i>	<i>a</i>										<u><i>abc</i></u>				<u><i>ae f</i></u>
<i>F</i>	<i>d</i>										<u><i>bcd</i></u>				<u><i>de f</i></u>
<i>F</i>	<i>bc</i>	<i>abc</i>			<i>bcd</i>										
<i>F</i>	<i>ef</i>	<i>ae f</i>			<i>de f</i>										
<i>G</i>	<i>ab</i>					<i>abe</i>							<i>abcd</i>		
<i>G</i>	<i>ac</i>					<i>ace</i>						<i>abcd</i>			
<i>G</i>	<i>ad</i>										<u><i>abcd</i></u>				<u><i>ade f</i></u>
<i>G</i>	<i>ae</i>	<i>abe</i>	<i>ace</i>								<i>abcd</i>			<i>ade f</i>	
<i>G</i>	<i>bd</i>						<i>bdf</i>		<i>abcd</i>						
<i>G</i>	<i>cd</i>						<i>cdf</i>	<i>abcd</i>							
<i>G</i>	<i>df</i>	<i>bdf</i>	<i>cdf</i>							<i>ade f</i>					

The co-kernel cube matrix is shown in Table 2, so the simplified *F* and *G* are

$$h = bc + ef$$

$$F = ah + dh + ce + be$$

$$G = adh + abe + ace + bdf + cdf$$

4 [Functional Dependency]

No, f_1 cannot be re-expressed with a function $h(y_2, y_3)$ for variables y_2 and y_3 being the output variables of f_2 and f_3 . The reason comes from the following two facts.

- (1) When $(a, b, c, d, e) = (0, 0, 1, 1, 0)$, $f_1 = 1$, $f_2 = 0$, and $f_3 = 1$.
- (2) When $(a, b, c, d, e) = (0, 1, 0, 0, 0)$, $f_1 = 0$, $f_2 = 0$, and $f_3 = 1$.

Therefore, given $(y_2, y_3) = (0, 1)$, we cannot decide whether f_1 is 0 or 1. In other words, the value of $h(0, 1)$ cannot be decided, so h cannot exist.

5 [SDC and ODC]

(a)

$$\begin{aligned}
 \text{SDC} &= (y_1 \oplus f_1) \vee (y_2 \oplus f_2) \vee (y_3 \oplus f_3) \vee (y_4 \oplus f_4) \vee (z_1 \oplus f_5) \vee (z_2 \oplus f_6) \\
 &= (y_1 \oplus (x_1 \vee \neg x_2)) \vee (y_2 \oplus \neg x_2 x_3) \vee (y_3 \oplus \neg x_3 \neg x_4) \\
 &\quad \vee (y_4 \oplus (\neg y_1 \neg y_2 \vee y_2 \neg y_3 \vee y_1 \neg y_3)) \vee (z_1 \oplus (y_1 \vee y_4)) \vee (z_2 \oplus (y_3 y_4))
 \end{aligned}$$

- (b) $SDC_4 = (y_1 \oplus (x_1 \vee \neg x_2)) \vee (y_2 \oplus \neg x_2 x_3) \vee (y_3 \oplus \neg x_3 \neg x_4)$. To make it depend on y_1, y_2, y_3 , the resulting formula is

$$\forall x_1, x_2, x_3, x_4. (SDC_4) = \neg y_1 y_2 \vee y_2 y_3.$$

(c)

$$ODC_{41} = \neg \frac{\partial z_1}{\partial y_4} = \neg(x_1 \vee \neg x_2 \oplus 1) = x_1 \vee \neg x_2$$

$$ODC_{42} = \neg \frac{\partial z_2}{\partial y_4} = \neg(0 \oplus \neg x_3 \neg x_4) = x_3 \vee x_4$$

$$ODC_4 = ODC_{41} \wedge ODC_{42} = (x_1 \vee \neg x_2) \wedge (x_3 \vee x_4)$$

6 [Don't Cares in Local Variables]

- (a) (5%) Compute the don't cares D_4 of Node 4 in terms of its local input variables y_1, y_2 , and y_3 . (Note that in general the computation of ODC may be affected by XDC especially when there exist different XDCs for different primary outputs.)

$$\begin{aligned} DC_4 &= (ODC_{41} \vee XDC_1) \wedge (ODC_{42} \vee XDC_2) \\ &= (x_1 \vee \neg x_2 \vee \neg x_1 \neg x_2 \neg x_3 \neg x_4) \wedge (x_3 \vee x_4 \vee x_1 x_2 \neg x_3 x_4) \\ &= (x_1 \vee \neg x_2) \wedge (x_3 \vee x_4) \\ D_4 &= \neg(\text{IMG}(\neg DC_4)) \\ &= \forall x_1, x_2, x_3, x_4. [(y_1 \oplus (x_1 \vee \neg x_2)) \vee (y_2 \oplus \neg x_2 x_3) \vee (y_3 \oplus \neg x_3 \neg x_4) \vee DC_4] \\ &= y_1 \neg y_3 \vee y_2 \end{aligned}$$

- (b) We can use K-map to minimize f_4 with don't cares D_4 , as shown below. The best implementable function for Node 4 is $f_4 = \neg y_1$.

$y_3 \setminus y_1 y_2$	00	01	11	10
0	1	x	x	x
1	1	x	x	0

7 [Complete Flexibility]

(a) (5%)

$$\begin{aligned}
f_5(X) &= f_1 \vee f_4 \\
&= f_1 \vee \neg f_1 \neg f_2 \vee f_2 \neg f_3 \vee f_1 \neg f_3 \\
&= (x_1 \vee \neg x_2) \vee (\neg x_1 x_2)(x_2 \vee \neg x_3) \vee (\neg x_2 x_3)(x_3 \vee x_4) \\
&= x_1 \vee \neg x_2 \vee \neg x_1 x_2 \\
&= 1 \\
f_6(X) &= f_3 f_4 \\
&= f_3(\neg f_1 \neg f_2 \vee f_2 \neg f_3 \vee f_1 \neg f_3) \\
&= f_3(\neg f_1 \neg f_2) \\
&= (\neg x_3 \neg x_4)(\neg x_1 x_2)(x_2 \vee \neg x_3) \\
&= \neg x_1 x_2 \neg x_3 \neg x_4 \\
S(X, Z) &= (\neg x_1 \neg x_2 \neg x_3 x_4 \vee (z_1 \Leftrightarrow f_5(X)))(x_1 x_2 \neg x_3 x_4 \vee (z_2 \Leftrightarrow f_6(X))) \\
&= (\neg x_1 \neg x_2 \neg x_3 x_4 \vee z_1)(x_1 x_2 \neg x_3 x_4 \vee (z_2 \Leftrightarrow \neg x_1 x_2 \neg x_3 \neg x_4))
\end{aligned}$$

(b)

$$I(X, y_4, Z) = (z_1 \Leftrightarrow (x_1 \vee \neg x_2 \vee y_4))(z_2 \Leftrightarrow (\neg x_3 \neg x_4 y_4))$$

(c)

$$E(X, Y) = (y_1 \Leftrightarrow (x_1 \vee \neg x_2))(y_2 \Leftrightarrow (\neg x_2 x_3))(y_3 \Leftrightarrow (\neg x_3 \neg x_4))$$

(d)

$$\begin{aligned}
CF(Y, y_4) &= \forall X, Z. [\neg(E(X, Y) \wedge I(X, y_4, Z) \wedge \neg S(X, Z))] \\
&= y_2 \vee y_1 \neg y_3 \vee y_1 \neg y_4 \vee \neg y_1 y_4 \vee \neg y_3 y_4
\end{aligned}$$

(e) Yes, D_4 is subsumed by CF_4 since $(D_4 \rightarrow CF_4)$ equals 1.

8 [Complete Flexibility for Multi-Nodes]

First, we have

$$\begin{aligned}
y_1 &= \neg x_1 x_2 \vee \neg x_1 x_3 \\
y_2 &= \neg x_1 \neg x_2 \neg x_3 \vee x_2 x_3 \\
z_1 &= \neg(y_1 \vee y_2) \\
&= x_1 \neg x_2 \vee x_1 \neg x_3 \\
z_2 &= \neg(y_1 \wedge y_2) \\
&= x_1 \vee \neg x_2 \vee \neg x_3 \\
S(X, Z) &= (z_1 \Leftrightarrow (x_1 \neg x_2 \vee x_1 \neg x_3))(z_2 \Leftrightarrow (x_1 \vee \neg x_2 \vee \neg x_3)) \\
I(X, y_1, y_2, Z) &= (z_1 \Leftrightarrow \neg y_1 \neg y_2)(z_2 \Leftrightarrow (\neg y_1 \vee \neg y_2))
\end{aligned}$$

Therefore,

$$\begin{aligned}
R(X, y_1, y_2) &= \forall Z. [I(X, y_1, y_2, Z) \rightarrow S(X, Z)] \\
&= \neg x_1 \neg x_2 \neg x_3 y_1 \neg y_2 \vee \neg x_1 \neg x_2 \neg x_3 \neg y_1 y_2 \vee \neg x_1 \neg x_2 x_3 y_1 \neg y_2 \\
&\vee \neg x_1 \neg x_2 x_3 \neg y_1 y_2 \vee \neg x_1 x_2 \neg x_3 \neg y_1 y_2 \vee \neg x_1 x_2 \neg x_3 y_1 \neg y_2 \\
&\vee \neg x_1 x_2 x_3 y_1 y_2 \vee x_1 \neg x_2 \neg x_3 \neg y_1 \neg y_2 \vee x_1 \neg x_2 x_3 \neg y_1 \neg y_2 \\
&\vee x_1 x_2 \neg x_3 \neg y_1 \neg y_2 \vee x_1 x_2 x_3 \neg y_1 y_2 \vee x_1 x_2 x_3 y_1 \neg y_2
\end{aligned}$$

We note that X are PIs of this circuit. Therefore, $CF(X, y_1, y_2)$ exactly equals $R(X, y_1, y_2)$ (see the proof below).

Then we can use K-map to minimize the circuit, as shown below, where a, b, c, d can be either 0 or 1. For example, $\neg x_1 \neg x_2 \neg x_3 y_1 \neg y_2$ and $\neg x_1 \neg x_2 \neg x_3 \neg y_1 y_2$ are both in $CF(X, y_1, y_2)$, so when $(x_1, x_2, x_3) = (0, 0, 0)$, the value of (y_1, y_2) can be either $(0, 1)$ or $(1, 0)$. Therefore, the $(0, 0, 0)$ entries of y_1 and y_2 are don't cares, but when assigning don't-care values to these two entries, y_1 and y_2 should be assigned with different values, and thereby we can assume $y_1 = a$ and $y_2 = \neg a$.

$x_3 \backslash x_1 x_2$		00	01	11	10
y_1 :	0	a	b	0	0
	1	c	1	d	0

$x_3 \backslash x_1 x_2$		00	01	11	10
y_2 :	0	$\neg a$	$\neg b$	0	0
	1	$\neg c$	1	$\neg d$	0

A best choice is $(a, b, c, d) = (1, 1, 1, 0)$, and the resulting simplified functions are $y_1 = \neg x_1$ and $y_2 = x_2 x_3$.

Proof of $CF(X, y_1, y_2) = R(X, y_1, y_2)$

We can imagine that the PIs of the network are $X_p = \{x_{1p}, x_{2p}, x_{3p}\}$, and X is connected to X_p through buffers. Therefore, $E(X, X_p) = (X \Leftrightarrow X_p)$, and $R(X_p, y_1, y_2) = (y_1 \Leftrightarrow (x_{1p}' x_{2p} + x_{1p}' x_{3p}))(y_2 \Leftrightarrow (x_{1p}' x_{2p}' x_{3p}' + x_{2p}' x_{3p}'))$. Then

$$\begin{aligned}
CF(X, y_1, y_2) &= \forall X_p. [E(X, X_p) \rightarrow R(X_p, y_1, y_2)] \\
&= [(X \Leftrightarrow 000) \rightarrow R(000, y_1, y_2)][(X \Leftrightarrow 001) \rightarrow R(001, y_1, y_2)] \\
&\quad [(X \Leftrightarrow 010) \rightarrow R(010, y_1, y_2)][(X \Leftrightarrow 011) \rightarrow R(011, y_1, y_2)] \\
&\quad [(X \Leftrightarrow 100) \rightarrow R(100, y_1, y_2)][(X \Leftrightarrow 101) \rightarrow R(101, y_1, y_2)] \\
&\quad [(X \Leftrightarrow 110) \rightarrow R(110, y_1, y_2)][(X \Leftrightarrow 111) \rightarrow R(111, y_1, y_2)].
\end{aligned}$$

We can find that whatever X is, we should replace X_p in $R(X_p, y_1, y_2)$ with the value of X . Therefore, $CF(X, y_1, y_2)$ exactly equals $R(X, y_1, y_2)$.